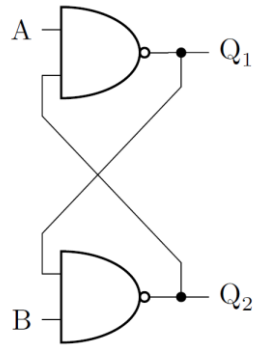


# MANAGEMENT AND ANALYSIS OF PHYSICS DATASET (MOD. A)

Memory Elements  
Sequential Circuits

# Memory elements

- If both inputs are at 1, the circuit keep memory of the previous state




<i>A</i>	<i>B</i>	<i>Q</i> <sub>2</sub>	<i>Q</i> <sub>1</sub>
0	0	1	1
1	0	1	0
0	1	0	1
1	1	<i>X</i>	$\overline{X}$

- Latch
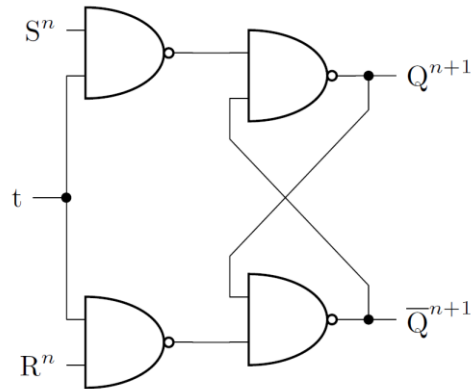
# Memory elements

- Flip-flop set-reset (S-R)
  - A synchronization input t is added
  - If t is not present the output doesn't change



$S^n$	$R^n$	$Q^{n+1}$	$\overline{Q}^{n+1}$
0	0	$Q^n$	$\overline{Q}^n$
1	0	1	0
0	1	0	1
1	1	-	-

$$Q^{n+1} = (Q \overline{S} \overline{R} + S \overline{R})^n = (S + Q \overline{R})^n$$
$$S R = 0$$

# Memory elements

- Flip-flop J-K
  - It removes the forbidden state
- Flip-flop D
  - Only one input
- How to build J-K and D?

$J^n$	$K^n$	$Q^{n+1}$	$\overline{Q}^{n+1}$
0	0	$Q^n$	$\overline{Q}^n$
1	0	1	0
0	1	0	1
1	1	$\overline{Q}^n$	$Q^n$

$$Q^{n+1} = (Q \overline{J} \overline{K} + J \overline{K} + \overline{Q} J K)^n = (Q \overline{K} + \overline{Q} J)^n$$


$D^n$	$Q^{n+1}$	$\overline{Q}^{n+1}$
0	0	1
1	1	0

$$Q^{n+1} = D^n$$

# Memory elements

- Usually, memory elements are controlled by logic functions

$a_0^n$	$a_1^n$	$Q^n$	$Q^{n+1}$	$S^n$	$R^n$	$J^n$	$K^n$	$D^n$
0	0	0	0	0	X	0	X	0
1	0	0	0	0	X	0	X	0
0	1	0	1	1	0	1	X	1
1	1	0	1	1	0	1	X	1
0	0	1	0	0	1	X	1	0
1	0	1	1	X	0	X	0	1
0	1	1	0	0	1	X	1	0
1	1	1	1	X	0	X	0	1

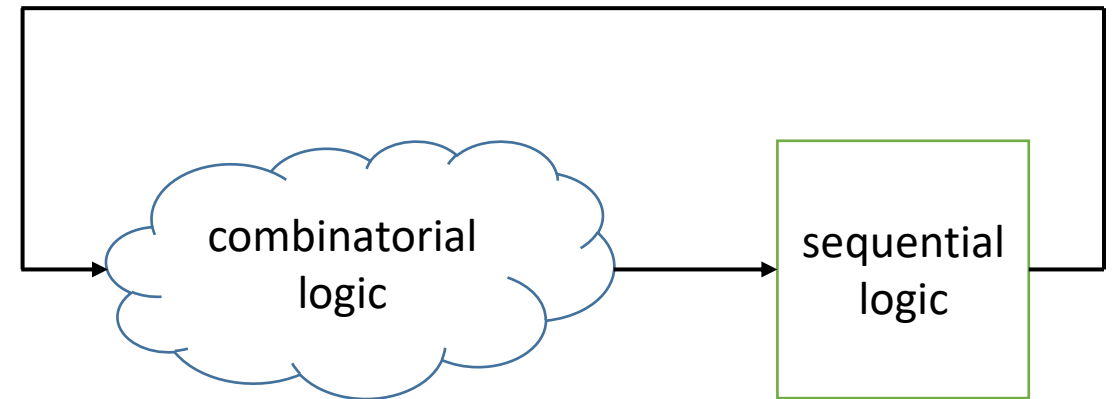

$$Q^{n+1} = (a_0 Q + a_1 \overline{Q})^n$$

$$S = a_1 \overline{Q}$$


$$R = \overline{a_0} Q$$

$$J = a_1$$


$$K = \overline{a_0}$$
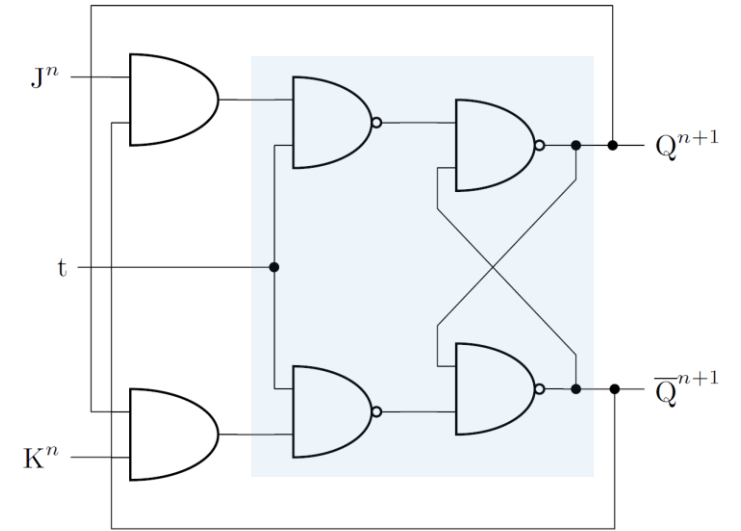
# Memory elements

$$\begin{array}{l} S = a_1 \bar{Q} \\ R = \bar{a}_0 Q \end{array} \quad \begin{array}{l} J = a_1 \\ K = \bar{a}_0 \end{array} \quad \Rightarrow \quad \begin{array}{l} S = J \bar{Q} \\ R = K Q \end{array}$$


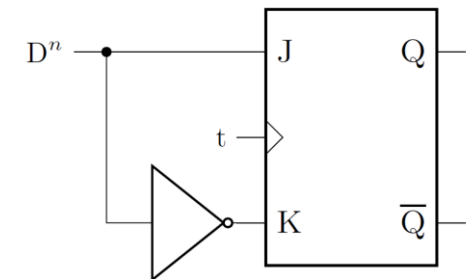
$$\begin{array}{l} J = a_1 \\ K = \bar{a}_0 \end{array} \quad D = a_0 Q + a_1 \bar{Q} \quad \Rightarrow \quad \begin{array}{l} J = D \\ K = \bar{D} \end{array}$$



# Exercises

- Make a J-K flip-flop from a D flip-flop
- Find the truth table of the flip-flop with the following equation
$$Q^{n+1} = [Q \oplus (M \oplus N)]^n$$
- Make the above flip-flop from a J-K flip-flop

# Counters and registers



# Decimal counter

- Design a 0-9 counter
- $A^{n+1} = \overline{A}^n$
- $B^{n+1} = [B(\overline{A}) + \overline{B}(A \overline{D})]^n$
- $C^{n+1} = [C(\overline{A} + \overline{B}) + \overline{C}(A B)]^n$
- $D^{n+1} = [D(\overline{A}) + \overline{D}(A B C)]^n$
- 4 FF J-K and 3 logic ports  
(assuming the complement of each variable is available)

$D^n$	$C^n$	$B^n$	$A^n$	$D^{n+1}$	$C^{n+1}$	$B^{n+1}$	$A^{n+1}$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

# Johnson counter

- It is a counter without switching incertitude because it changes only one bit at a time
- $m$ -bit Johnson counter  $\rightarrow$  sequence of  $2m$  numbers
- If we use the redundant terms, we get

$$A^{n+1} = \overline{C^n}$$

$$B^{n+1} = A^n$$

$$C^{n+1} = B^n$$

- It nicely corresponds to a D flip-flop chain, but if the system starts by chance from a redundant term, it never get out!
- We need to avoid that making the schematics a little bit more complex

$$A^{n+1} = \overline{C^n}$$



$$B^{n+1} = [A(B + \overline{C})]^n$$

$$C^{n+1} = B^n$$

$A^n$	$B^n$	$C^n$	$A^{n+1}$	$B^{n+1}$	$C^{n+1}$
0	0	0	1	0	0
1	0	0	1	1	0
1	1	0	1	1	1
1	1	1	0	1	1
0	1	1	0	0	1
0	0	1	0	0	0

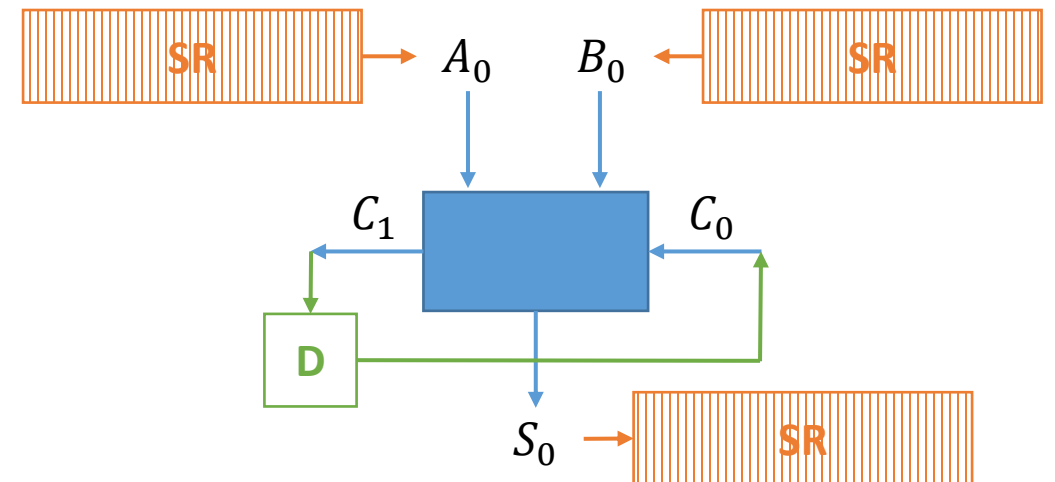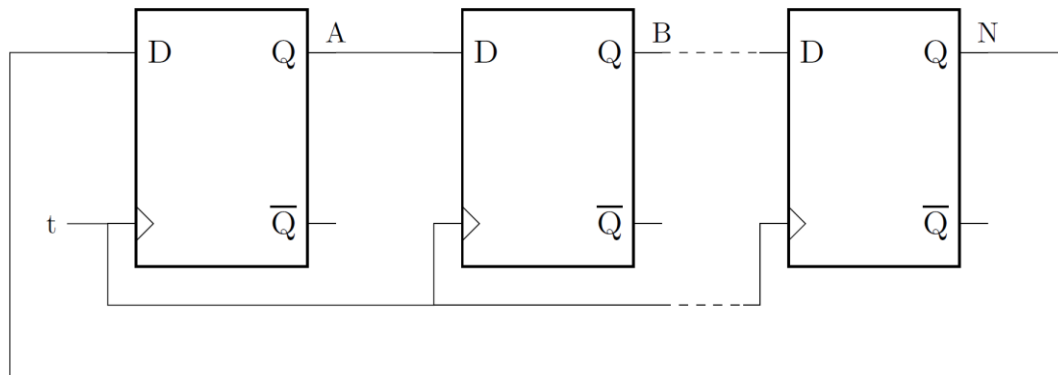
# Shift register

- It is used to shift a signal
- Its design can be obtained by the sequential table
- Without feedback can be used to access in parallel to a serial data or to serialize a parallel data
- Each cell can have a multiplexer to choose if shifting the bit or loading a new bit


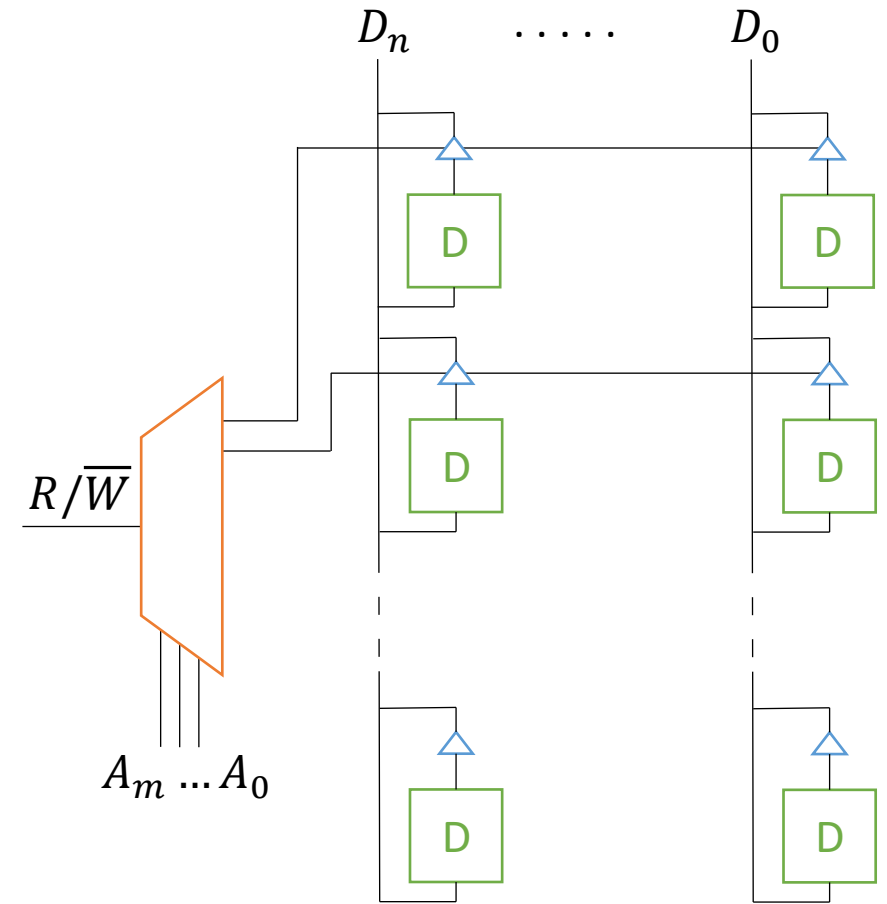
# Memory

- It can be seen as an array of FF
- A decoder is used for addressing the data row
- A tristate allows read/write operation
- Memory size = data width  $\times 2^{\text{address width}}$
- Random Access Memory (RAM)
  - If Read Only is called ROM
  - It can contain a truth table -> It implements any combinatorial function (one for each data bit)




# Exercises

- Design a 4-bit down counter
- Design an  $n$ -bit shift register that starts from a state where all the bits are equal to zero:  $00\dots0 \rightarrow 10\dots0 \rightarrow 01\dots0$ , etc.

State machines

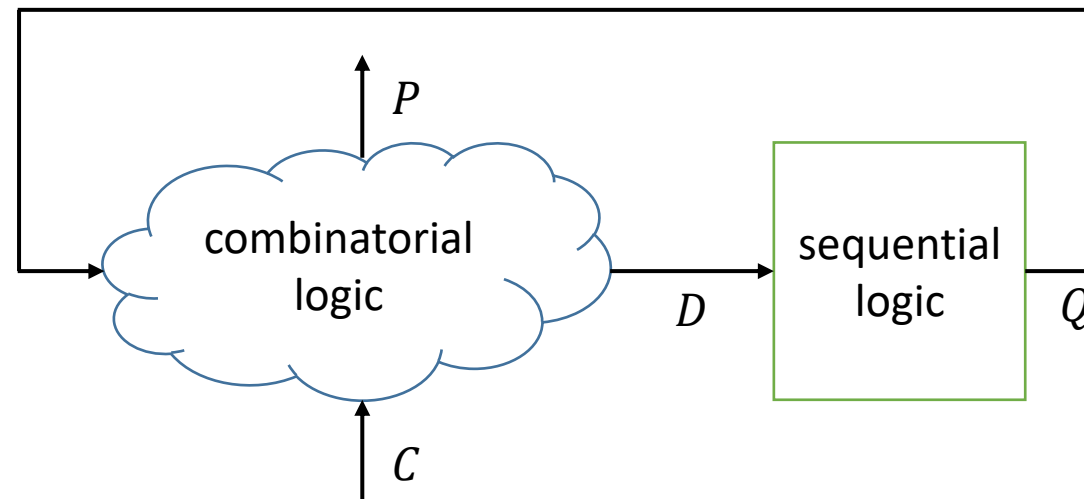
# State machine

- A general schema for functions that control sequential logic take into account external signals  $C$  and produce control signals  $P$ 
  - Mealey state machine:  $P$  is function of  $C$  and  $Q$
  - Moore state machine:  $P$  is only function of  $Q$
- Moore outputs are synchronous


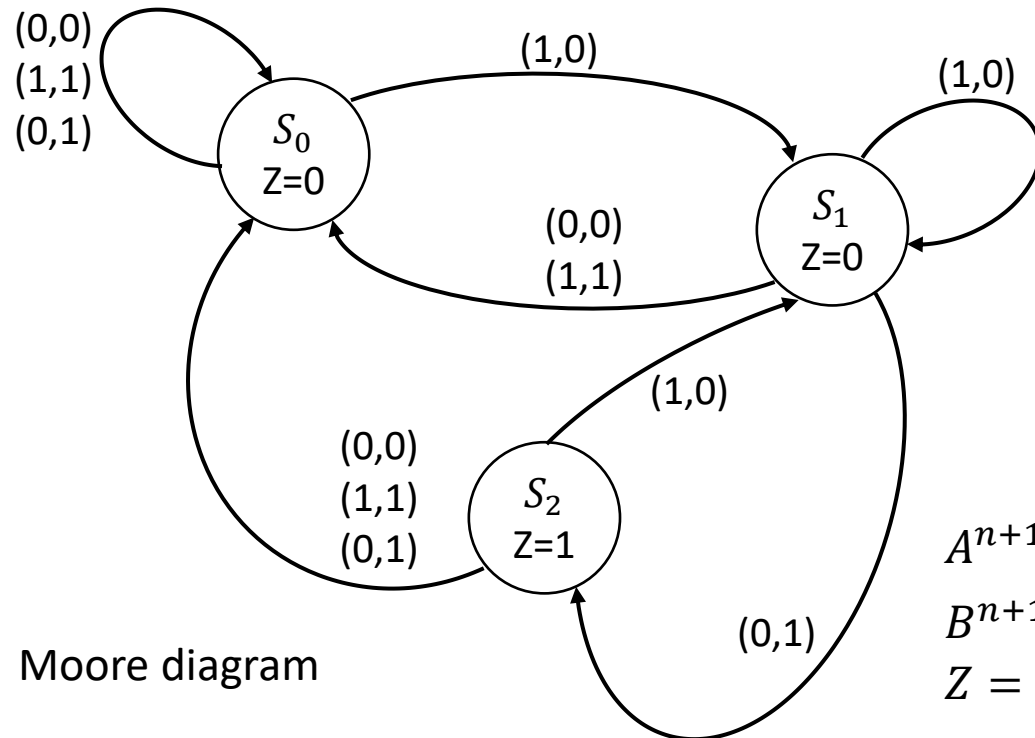
# State machine

- Find the transition (1,0) -> (0,1) of two bits (M,N)



$$A^{n+1} = (M \overline{N})^n$$
$$B^{n+1} = (A \overline{M} N)^n$$
$$Z = B$$


<i>M</i>	<i>N</i>	$A^n$	$B^n$	$A^{n+1}$	$B^{n+1}$	<i>Z</i>
0	0	0	0	0	0	0
1	0	0	0	1	0	0
0	1	0	0	0	0	0
1	1	0	0	0	0	0
0	0	1	0	0	0	0
1	0	1	0	1	0	0
0	1	1	0	0	1	1
1	1	1	0	0	0	0
0	0	0	1	0	0	0
1	0	0	1	1	0	0
0	1	0	1	0	0	0
1	1	0	1	0	0	0


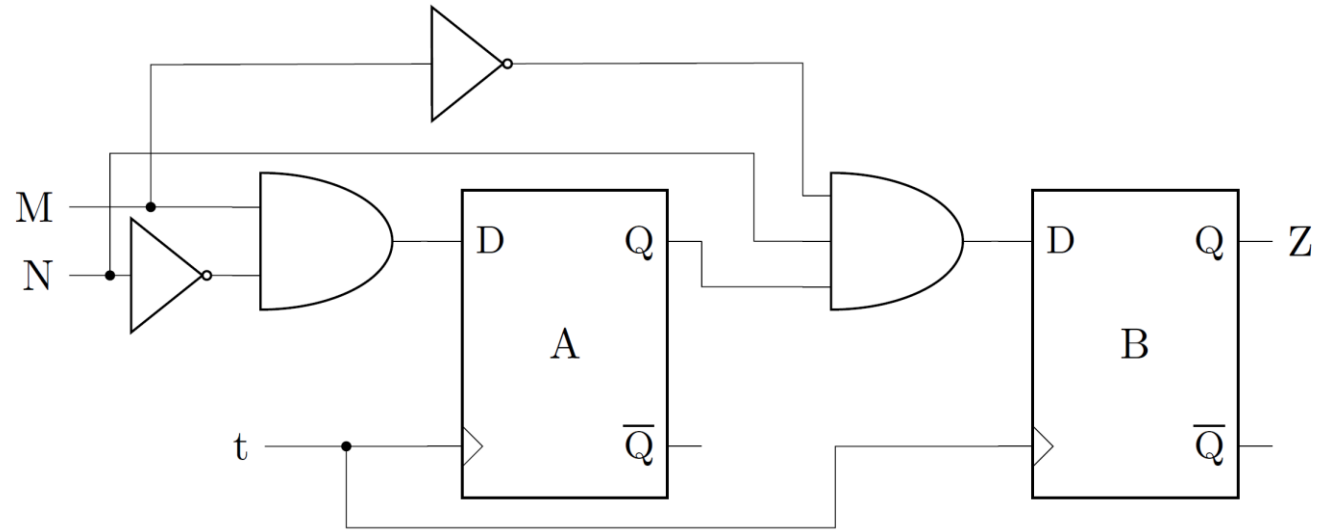
# State machine


- Find the transition  $(1,0) \rightarrow (0,1)$  of two bits  $(M,N)$

$$A^{n+1} = (M \overline{N})^n$$
$$B^{n+1} = (A \overline{M} N)^n$$
$$Z = B$$


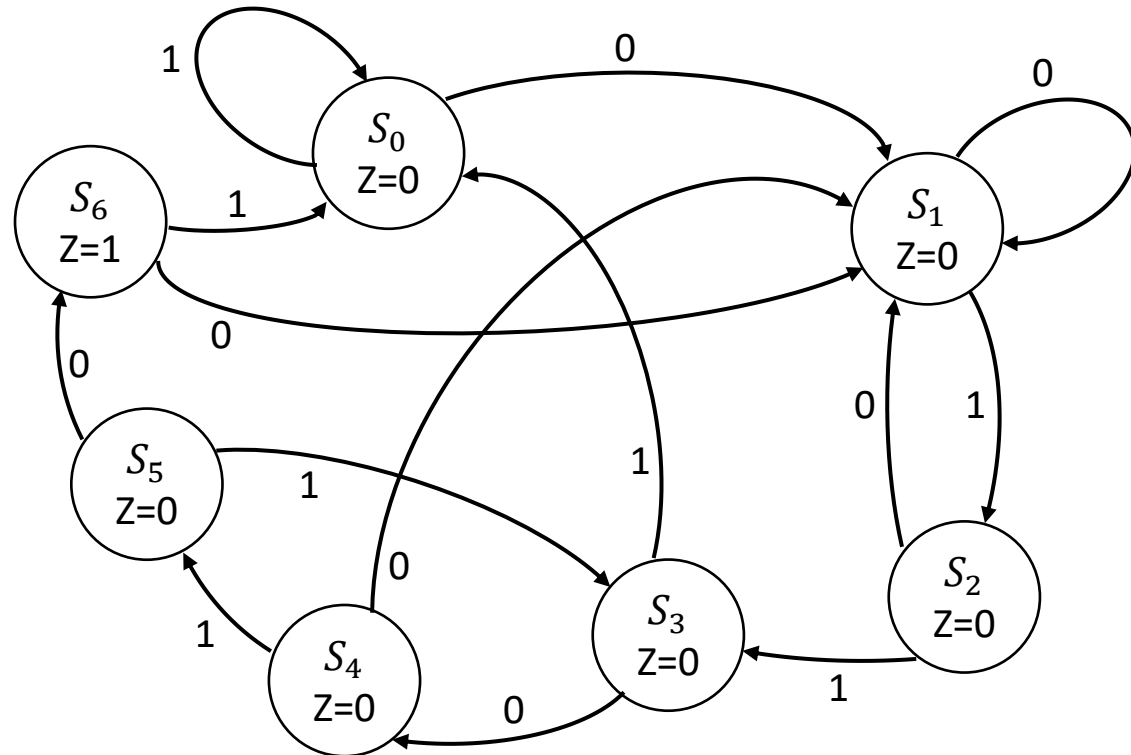
# State machine

- Find the sequence ...011010... on a data line  $M$



$M$	$A^n$	$B^n$	$C^n$	$A^{n+1}$	$B^{n+1}$	$C^{n+1}$
0	0	0	0	1	0	0
1	0	0	0	0	0	0
0	1	0	0	1	0	0
1	1	0	0	0	1	0
0	0	1	0	1	0	0
1	0	1	0	1	1	0
0	1	1	0	0	0	1
1	1	1	0	0	0	0
0	0	0	1	1	0	0
1	0	0	1	1	0	1
0	1	0	1	0	1	1
1	1	0	1	1	1	0
0	0	1	1	1	0	0
1	0	1	1	0	0	0

# Exercises

- Complete the previous example designing the state machine circuit with the use of J-K flip-flops
- Design a controller for an elevator
  - The elevator can be at one of the three floors: Ground, First and Second
  - There is a button that controls the elevator, and it has two possible values: up and down
  - The elevator goes up one floor every time you set the button to “up”, and goes down one floor every time you set the button to “down”
  - There are two lights in a row in the elevator that indicate the current floor: both lights off (00) indicates the ground floor; the left light off and right light on (01) indicates the first floor; the right light off and left light on (10) indicates the second floor