

# MANAGEMENT AND ANALYSIS OF PHYSICS DATASET (MOD. A)

Fundamentals of Boolean Algebra  
Combinatorial Functions

# Postulates of the Boolean algebra





- Digital circuits or logic circuits deal with quantized signals (lack or presence of a signal)
- Fundamental elements of the digital computing
- “Logic” because we can apply analysis and synthesis methods derived from Boolean algebra
- Class of elements  $M$  and two operators  $\cdot$  and  $+$

P1:	$A + B = B + A$	$AB = BA$	Commutative
P2:	$A + 0 = A$	$A \cdot 1 = A$	Identity
P3:	$A + \bar{A} = 1$	$A\bar{A} = 0$	Complement
P4:	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$	Distributive


- Duality of the operators
    
# Postulates of the Boolean algebra

- Proof of non contradiction:  $\cdot$  are connections,  $\cdot$  is the circuital operator AND and  $+$  is the OR





A	B	AB
0	0	0
1	0	0
0	1	0
1	1	1

 


A	B	A+B
0	0	0
1	0	1
0	1	1
1	1	1
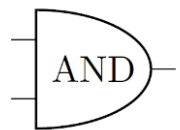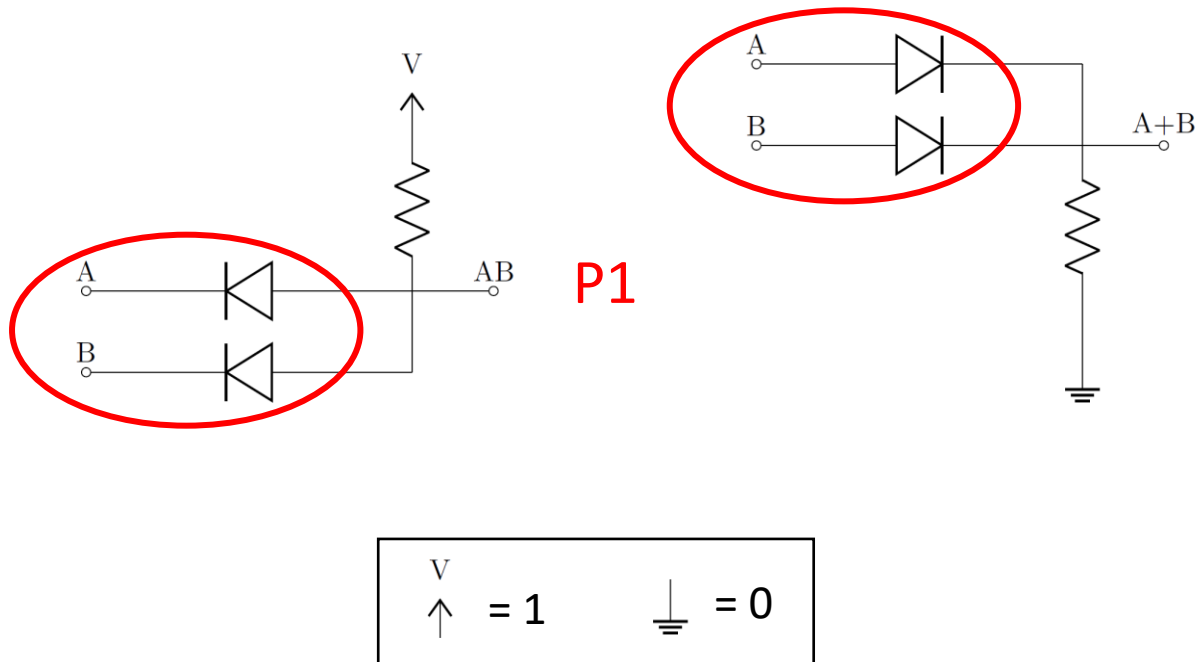
# Postulates of the Boolean algebra

- Proof of non contradiction:  $\cdot$  are connections,  $\cdot$  is the circuital operator AND and  $+$  is the OR







A	B	AB
0	0	0
1	0	0
0	1	0
1	1	1

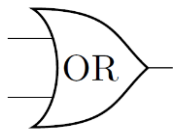


A	B	A+B
0	0	0
1	0	1
0	1	1
1	1	1
    
# Postulates of the Boolean algebra

- Proof of non contradiction:  $\cdot$  are connections,  $\cdot$  is the circuital operator AND and  $+$  is the OR



A	B	AB
0	0	0
1	0	0
0	1	0
1	1	1





 


A	B	A+B
0	0	0
1	0	1
0	1	1
1	1	1

P2
     
# Postulates of the Boolean algebra

- Proof of non contradiction:  $\cdot$  are connections,  $\cdot$  is the circuital operator AND and  $+$  is the OR



A	B	AB
0	0	0
1	0	0
0	1	0
1	1	1

A	B	A+B
0	0	0
1	0	1
0	1	1
1	1	1


P3

# Postulates of the Boolean algebra


- Proof of non contradiction:  $\cdot$  are connections,  $\cdot$  is the circuitual operator AND and  $+$  is the OR

P4

A	B	C	A+BC	(A+B)(A+C)
0	0	0	0	0
1	0	0	1	1
0	1	0	0	0
1	1	0	1	1
0	0	1	0	0
1	0	1	1	1
0	1	1	1	1
1	1	1	1	1

 



A	B	AB
0	0	0
1	0	0
0	1	0
1	1	1

 

A	B	A+B
0	0	0
1	0	1
0	1	1
1	1	1
  
# Postulates of the Boolean algebra

- The postulates are valid also for other classes
- For instance:  $M$  is the class of all subsets of the set  $M$ ,  $\cdot$  is the intersection and  $+$  is the union
- Graphical representation can be used to quickly proof theorems





# Simple theorems

T1:  $A + A = A$

$$AA = A$$

Proof:  $A + A = (A + A) \cdot 1 = (A + A)(A + \bar{A}) = A + A\bar{A} = A + 0 = A$

T2:  $A + 1 = 1$

$$A \cdot 0 = 0$$

Proof:  $A + 1 = (A + 1) \cdot 1 = (A + 1)(A + \bar{A}) = A + \bar{A} \cdot 1 = A + \bar{A} = 1$

T3:  $A + AB = A$

$$A(A + B) = A$$

Proof:  $A + AB = (A \cdot 1) + AB = A(1 + B) = A \cdot 1 = A$

# De Morgan laws

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

Proof:

$$(A + B) + \overline{A} \cdot \overline{B} = (A + B + \overline{A})(A + B + \overline{B}) = (B + 1)(A + 1) = 1 \cdot 1 = 1$$

$$(A + B) \cdot \overline{A} \cdot \overline{B} = A \cdot \overline{A} \cdot \overline{B} + B \cdot \overline{A} \cdot \overline{B} = \overline{B} \cdot 0 + \overline{A} \cdot 0 = 0 + 0 = 0$$

From P3 we can conclude that  $A+B$  is the complementary of  $\overline{A} \cdot \overline{B}$

Generalization: the complementary of a Boolean function results from the exchange of the dual operators and from the exchange of the operands with their complement

# Exercises

1. Demonstrate that  $(A + B)(\overline{A} + C) = \overline{A}B + AC$
2. Demonstrate that  $f(A, B) = \overline{A} \overline{B} + AB = \overline{f}(\overline{A}, B)$

# Combinatorial functions

# Combinatorial functions

- A simple way of describing a Boolean function is the truth table

A	B	$f(A, B) = \overline{A} + \overline{B}$
0	0	1
1	0	1
0	1	1
1	1	0

- It describes  $f$  as function of its input -> combinatory function
- Many functions can be built from the same truth table

$$\begin{aligned} f(A, B) &= \overline{A \cdot B} \\ &= \overline{A} \overline{B} + \overline{A} B + A \overline{B} \\ &= \overline{B} + \overline{A} B \end{aligned}$$

*Which is the best?*

# Canonical form

- Minterm ( $m$ ) of  $n$  variables is the Boolean product of all the variables where they appears only once (either in the complemented or uncomplemented form)
- They are  $2^n$ . For instance, for  $n = 2$  they are  $\bar{A} \bar{B}$ ,  $A \bar{B}$ ,  $\bar{A} B$  and  $A B$
- Similarly, Maxterm ( $M$ ) can be defined for the sum

A	B	Minterm	Maxterm
0	0	$m_0 = \bar{A} \bar{B}$	$M_0 = \bar{A} + \bar{B}$
1	0	$m_1 = A \bar{B}$	$M_1 = A + \bar{B}$
0	1	$m_2 = \bar{A} B$	$M_2 = \bar{A} + B$
1	1	$m_3 = A B$	$M_3 = A + B$

# Canonical form

- $m_i$  is always equal to 0 except in one case (variables in line  $i$ )
- $M_i$  is always equal to 1 except in one case (variables in line  $2^n - 1 - i$ )
- The product of two distinct minterms is always 0 and the sum of two distinct maxterm is always 1

$$\overline{m_i} = M_{2^n-1-i}$$

$$\overline{M_i} = m_{2^n-1-i}$$

$$\sum_{i=0}^{2^n-1} m_i = 1$$

$$\prod_{i=0}^{2^n-1} M_i = 0$$

# Canonical form

- Combinatorial functions expressed as a sum of minterms or product of maxterms are said to be in canonical form

A	B	$f(A, B) = \overline{A} + \overline{B}$
0	0	1
1	0	1
0	1	1
1	1	0

A	B	$F_k$
0	0	$f_0$
1	0	$f_1$
0	1	$f_2$
1	1	$f_3$

$$f(A, B) = m_0 + m_1 + m_2$$

$$f(A, B) = M_0$$

$$F_k = \sum_{i=0}^{2^n-1} f_i m_i$$

$$F_k = \prod_{i=0}^{2^n-1} (f_i + M_{2^n-1-i})$$



# Canonical form

- All the possible Boolean function of  $n$  variables are  $2^{2^n}$


$f_0$	$f_1$	$f_2$	$f_3$	$F_k$
0	0	0	0	<b>0</b>
1	0	0	0	$NOR$
0	1	0	0	$A\overline{B}$
1	1	0	0	$\overline{B}$
0	0	1	0	$\overline{A}B$
1	0	1	0	$\overline{A}$
0	1	1	0	$XOR$
1	1	1	0	$NAND$
0	0	0	1	$AND$
1	0	0	1	$\overline{XOR}$
0	1	0	1	$A$
1	1	0	1	$A + \overline{B}$
0	0	1	1	$B$
1	0	1	1	$\overline{A} + B$
0	1	1	1	$OR$
1	1	1	1	<b>1</b>

# From function to circuit

- Canonical form is the most generic, but it is not the simplest
- For building a circuit it is better to simplify
- Passive circuits cannot be used because they degrades the signal after few logic levels -> active components at least in the output stage
- The simplest amplifier is the common emitter transistor -> signal inversion -> NAND or NOR
- Any combinatorial Boolean function can be written with them
  - The complement of a variable is done wiring together the two inputs or applying a 1 for NAND and 0 for NOR
  - By De Morgan NAND is the OR of complements and NOR is the AND of complements


# From function to circuit

$$f = A B + \bar{A} \bar{B}$$

 


Sum of products

$$f = (A + \bar{B})(\bar{A} + B)$$

 


Product of sums

 

De Morgan duality
 
# XOR

- $A \oplus B = \bar{A} \oplus \bar{B} = A \bar{B} + \bar{A} B$
- $\overline{A \oplus B} = \bar{A} \oplus B = \bar{A} \bar{B} + A B$



- $\bar{A} = 1 \oplus A$
- $A + B = \overline{\bar{A} \bar{B}} = 1 \oplus [(1 \oplus A)(1 \oplus B)]$
- $A B = \overline{\bar{A} + \bar{B}} = 1 \oplus [(1 \oplus A) + (1 \oplus B)]$

A	B	$A \oplus B$
0	0	0
1	0	1
0	1	1
1	1	0

# Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

	A	
B	$m_3$	$m_2$
	$m_1$	$m_0$

	-----A-----			
B	$m_3$	$m_7$	$m_6$	$m_2$
	$m_1$	$m_5$	$m_4$	$m_0$
	-----C-----			

	-----A-----			
B	$m_3$	$m_7$	$m_6$	$m_2$
	$m_{11}$	$m_{15}$	$m_{14}$	$m_{10}$
	$m_9$	$m_{13}$	$m_{12}$	$m_8$
	$m_1$	$m_5$	$m_4$	$m_0$
	-----C-----			
				D

# Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

	A	
B	$m_3$	$m_2$
	$m_1$	$m_0$

$$m_0 = \overline{A}\overline{B}$$

	A			
B	$m_3$	$m_7$	$m_6$	$m_2$
	$m_1$	$m_5$	$m_4$	$m_0$

	A			
B	$m_3$	$m_7$	$m_6$	$m_2$
	$m_{11}$	$m_{15}$	$m_{14}$	$m_{10}$
	$m_9$	$m_{13}$	$m_{12}$	$m_8$
	$m_1$	$m_5$	$m_4$	$m_0$
C				D

# Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

	A	
B	$m_3$	$m_2$
	$m_1$	$m_0$

$$m_1 = A\bar{B}$$

	-----A-----			
B	$m_3$	$m_7$	$m_6$	$m_2$
	$m_1$	$m_5$	$m_4$	$m_0$
	-----C-----			

	-----A-----			
B	$m_3$	$m_7$	$m_6$	$m_2$
	$m_{11}$	$m_{15}$	$m_{14}$	$m_{10}$
	$m_9$	$m_{13}$	$m_{12}$	$m_8$
	$m_1$	$m_5$	$m_4$	$m_0$
	-----C-----			
				D

# Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

A	
B	$m_3$
	$m_2$
	$m_1$
	$m_0$

$$m_2 = \bar{A}B$$

A			
B	$m_3$	$m_7$	$m_6$
	$m_2$	$m_1$	$m_5$
	$m_4$	$m_0$	
C			

A			
B	$m_3$	$m_7$	$m_6$
	$m_2$	$m_{11}$	$m_{15}$
	$m_{14}$	$m_{10}$	$m_9$
	$m_{13}$	$m_{12}$	$m_8$
	$m_1$	$m_5$	$m_4$
	$m_0$		
C			
D			



# Graphical simplification

- A function is represented as union of intersections of subsets
- Veitch or Karnaugh maps

A	
B	$m_3$
	$m_2$
	$m_1$
	$m_0$

$$m_3 = AB$$

A			
B	$m_3$	$m_7$	$m_6$
	$m_2$	$m_5$	$m_4$
	$m_1$	$m_0$	
C			

A			
B	$m_3$	$m_7$	$m_6$
	$m_{11}$	$m_{15}$	$m_{14}$
	$m_9$	$m_{13}$	$m_{12}$
	$m_1$	$m_5$	$m_4$
	$m_0$		
C			
D			

# Graphical simplification

- $f = \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}B\overline{C}\overline{D} + AB\overline{C}\overline{D} + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + A\overline{B}CD + ABCD$

-----A-----				
-----B-----	$m_3$	$m_7$	$m_6$	$m_2$
	$m_{11}$	$m_{15}$	$m_{14}$	$m_{10}$
	$m_9$	$m_{13}$	$m_{12}$	$m_8$
	$m_1$	$m_5$	$m_4$	$m_0$
-----C-----				-----D-----

# Graphical simplification

- $f = \overline{A} \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B C \overline{D} + A \overline{B} C D + A B C D$

- $f = AC + \overline{C} \overline{D}$  -> NAND

$m_3$	$m_7$	$m_6$	$m_2$
$m_{11}$	$m_{15}$	$m_{14}$	$m_{10}$
$m_9$	$m_{13}$	$m_{12}$	$m_8$
$m_1$	$m_5$	$m_4$	$m_0$

# Graphical simplification

- $f = \overline{A} \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B C \overline{D} + A \overline{B} C D + A B C D$
- $f = A C + \overline{C} \overline{D} \rightarrow \text{NAND}$

A 4x4 Karnaugh map for the function f(A, B, C, D). The map is a 4x4 grid of cells, each labeled with a minterm m<sub>i</sub>. The cells are shaded gray if they are part of the function f, and white otherwise. The shaded cells are m<sub>3</sub>, m<sub>7</sub>, m<sub>15</sub>, m<sub>13</sub>, m<sub>5</sub>, m<sub>1</sub>, m<sub>0</sub>, and m<sub>2</sub>. The unshaded cells are m<sub>6</sub>, m<sub>11</sub>, m<sub>14</sub>, m<sub>10</sub>, m<sub>9</sub>, m<sub>12</sub>, m<sub>8</sub>, and m<sub>4</sub>. The map is labeled with variables A, B, C, and D. A is at the top, B is on the left, C is at the bottom, and D is on the right. The map is a 4x4 grid of cells, each labeled with a minterm m<sub>i</sub>. The cells are shaded gray if they are part of the function f, and white otherwise. The shaded cells are m<sub>3</sub>, m<sub>7</sub>, m<sub>15</sub>, m<sub>13</sub>, m<sub>5</sub>, m<sub>1</sub>, m<sub>0</sub>, and m<sub>2</sub>. The unshaded cells are m<sub>6</sub>, m<sub>11</sub>, m<sub>14</sub>, m<sub>10</sub>, m<sub>9</sub>, m<sub>12</sub>, m<sub>8</sub>, and m<sub>4</sub>. The map is labeled with variables A, B, C, and D. A is at the top, B is on the left, C is at the bottom, and D is on the right.

	-----A-----			
-----B-----	$m_3$	$m_7$	$m_6$	$m_2$
	$m_{11}$	$m_{15}$	$m_{14}$	$m_{10}$
	$m_9$	$m_{13}$	$m_{12}$	$m_8$
	$m_1$	$m_5$	$m_4$	$m_0$
	-----C-----			
				-----D-----

# Graphical simplification

- $f = \overline{A} \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B C \overline{D} + A \overline{B} C D + A B C D$
- $f = A C + \overline{C} \overline{D} \rightarrow \text{NAND}$
- $\overline{f} = \overline{A} C + \overline{C} D$
- $f = (A + \overline{C})(C + \overline{D}) \rightarrow \text{NOR}$

A 4x4 Karnaugh map for variables A, B, C, and D. The map is organized with A as the column index (0 to 3) and B as the row index (0 to 3). The cells are labeled with minterms m<sub>0</sub> through m<sub>15</sub>. The cells are colored as follows: m<sub>6</sub>, m<sub>14</sub>, and m<sub>4</sub> are green; m<sub>11</sub>, m<sub>15</sub>, m<sub>9</sub>, m<sub>10</sub>, m<sub>8</sub>, and m<sub>3</sub> are blue; all other cells (m<sub>7</sub>, m<sub>2</sub>, m<sub>13</sub>, m<sub>5</sub>, m<sub>1</sub>, m<sub>0</sub>) are gray. Dashed lines indicate the variable axes: A (horizontal, top), B (vertical, left), C (horizontal, bottom), and D (vertical, right).

	-----A-----			
-----B-----	m <sub>3</sub>	m <sub>7</sub>	m <sub>6</sub>	m <sub>2</sub>
	m <sub>11</sub>	m <sub>15</sub>	m <sub>14</sub>	m <sub>10</sub>
	m <sub>9</sub>	m <sub>13</sub>	m <sub>12</sub>	m <sub>8</sub>
	m <sub>1</sub>	m <sub>5</sub>	m <sub>4</sub>	m <sub>0</sub>
	-----C-----			-----D-----

# Exercises

1. Demonstrate that  $(A \oplus B) \oplus C = A \oplus (B \oplus C) = B \oplus (A \oplus C)$
2. Simplify  $AB\bar{C} + ABC + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + \bar{A}\bar{B}C$

Examples of combinatorial logic

# Adder

- Elementary cell for adding two bits (binary digit)
- Extension to two n-bits numbers

$A_i$	$B_i$	$C_i$	$S_i$	$C_{i+1}$
0	0	0	0	0
1	0	0	1	0
0	1	0	1	0
1	1	0	0	1
0	0	1	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

$$S_i = (A \bar{B} \bar{C} + \bar{A} B \bar{C} + \bar{A} \bar{B} C + A B C)_i$$

$$C_{i+1} = (A B \bar{C} + A \bar{B} C + \bar{A} B C + A B C)_i$$


$$S_i = (A \bar{B} + \bar{A} B)_i \bar{C}_i + (\bar{A} \bar{B} + A B)_i C_i = (A \oplus B)_i \oplus C_i$$

$$C_{i+1} = (A B + A C + B C)_i$$


 
# Adder

- Elementary cell for adding two bits (binary digit)
- Extension to two n-bits numbers



$$S_i = (A \overline{B} \overline{C} + \overline{A} B \overline{C} + \overline{A} \overline{B} C + A B C)_i$$



$$C_{i+1} = (A B \overline{C} + A \overline{B} C + \overline{A} B C + A B C)_i$$

$$S_i = (A \overline{B} + \overline{A} B)_i \overline{C}_i + (\overline{A} \overline{B} + A B)_i C_i = (A \oplus B)_i \oplus C_i$$

$$C_{i+1} = (A B + A C + B C)_i$$
  
# Adder

- Elementary cell for adding two bits (binary digit)
- Extension to two n-bits numbers



# Subtractor

- Exercise
  - Draw the circuit
  - Can be easily obtained from an adder?

# Subtractor

$A_i$	$B_i$	$R_i$	$D_i$	$R_{i+1}$
0	0	0	0	0
1	0	0	1	0
0	1	0	1	1
1	1	0	0	0
0	0	1	1	1
1	0	1	0	0
0	1	1	0	1
1	1	1	1	1


$$D_i = (A \bar{B} \bar{R} + \bar{A} B \bar{R} + \bar{A} \bar{B} R + A B R)_i$$

$$R_{i+1} = (\bar{A} B \bar{R} + \bar{A} \bar{B} R + \bar{A} B R + A B R)_i$$

$$D_i = (A \bar{B} + \bar{A} B)_i \bar{R}_i + (\bar{A} \bar{B} + A B)_i R_i = (A \oplus B)_i \oplus R_i$$

$$R_{i+1} = (\bar{A} B + \bar{A} R + B R)_i$$

# Subtractor

 

$$D_i = (A \bar{B} \bar{R} + \bar{A} B \bar{R} + \bar{A} \bar{B} R + A B R)_i$$

$$R_{i+1} = (\bar{A} B \bar{R} + \bar{A} \bar{B} R + \bar{A} B R + A B R)_i$$

$$D_i = (A \bar{B} + \bar{A} B)_i \bar{R}_i + (\bar{A} \bar{B} + A B)_i R_i = (A \oplus B)_i \oplus R_i$$

$$R_{i+1} = (\bar{A} B + \bar{A} R + B R)_i$$

# Adder

- Modular adder has a propagation delay that depends on the number of bits ( $n$ )
- Carry propagation delay:  $2T_P \cdot n$
- Carry can be calculated in parallel
- Carry-lookahead
  - Generate a carry if  $A$  and  $B$  are 1:  $G_i = A_i B_i$
  - Propagate a carry if  $A$  or  $B$  are 1:  $P_i = A_i + B_i$  but also if  $P_i = A_i \oplus B_i$
- $C_{i+1} = G_i + C_i P_i$
- $C_4 = A_3 B_3 + A_2 B_2 (A_3 \oplus B_3) + A_1 B_1 (A_2 \oplus B_2) (A_3 \oplus B_3) + A_0 B_0 (A_1 \oplus B_1) (A_2 \oplus B_2) (A_3 \oplus B_3) + C_0 (A_0 \oplus B_0) (A_1 \oplus B_1) (A_2 \oplus B_2) (A_3 \oplus B_3)$
- Parallel carry propagation delay:  $3T_P$

# Parity generator

- The parity bit is a bit that added to the data makes the total number of ones (1s) even (even parity) or odd (odd parity)
- Parity is used for error detection during data transmission
- For instance, 1001010 has  $P_{odd} = 0$  and  $P_{even} = 1$
- Elementary cell for odd parity generation
- Extension to two n-bits numbers


$D_i$	$P_i$	$P_{i+1}$
0	0	0
1	0	1
0	1	1
1	1	0

$$P_{i+1} = (D \bar{P} + \bar{D} P)_i = (D \oplus P)_i$$

$$P_0 = 1$$
 
# Parity generator


- The parity bit is a bit that added to the data makes the total number of ones (1s) even (even parity) or odd (odd parity)
- Parity is used for error detection during data transmission
- For instance, 1001010 has  $P_{odd} = 0$  and  $P_{even} = 1$
- Elementary cell for odd parity generation
- Extension to two n-bits numbers




 
# Parity generator

- And for even parity generator?
  - Just change  $P_0$
- As for the adder we can limit the propagation time with a module that works in parallel
- It is possible to connect the single module in a tree-like structure




$$P = (D_0 \oplus D_1) \oplus (D_2 \oplus D_3)$$

# Comparison

- For comparing two binary numbers  $(a, b)$ , three output values are needed -> two output bits  $(N, M)$
- Modular approach for n-bits extension

	$N$	$M$
$a > b$	0	1
$a < b$	1	0
$a = b$	0	0

 


$a_i$	$b_i$	$N_{i+1}$	$M_{i+1}$	$N_i$	$M_i$
0	0	0	0	0	0
1	0	0	0	0	1
0	1	0	0	1	0
1	1	0	0	0	0
0	0	1	0	1	0
1	0	1	0	1	0
0	1	1	0	1	0
1	1	1	0	1	0
0	0	0	1	0	1
1	0	0	1	0	1
0	1	0	1	0	1
1	1	0	1	0	1
0	0	1	1	X	X
1	0	1	1	X	X
0	1	1	1	X	X
1	1	1	1	X	X

# Comparison

- For comparing two binary numbers  $(a, b)$ , three output values are needed  $\rightarrow$  two output bits  $(N, M)$
- Modular approach for n-bits extension

	$N$	$M$
$a > b$	0	1
$a < b$	1	0
$a = b$	0	0

 

Redundant terms

$a_i$	$b_i$	$N_{i+1}$	$M_{i+1}$	$N_i$	$M_i$
0	0	0	0	0	0
1	0	0	0	0	1
0	1	0	0	1	0
1	1	0	0	0	0
0	0	1	0	1	0
1	0	1	0	1	0
0	1	1	0	1	0
1	1	1	0	1	0
0	0	0	1	0	1
1	0	0	1	0	1
0	1	0	1	0	1
1	1	0	1	0	1
0	0	1	1	X	X
1	0	1	1	X	X
0	1	1	1	X	X
1	1	1	1	X	X

# Comparison

- For comparing two binary numbers  $(a, b)$ , three output values are needed -> two output bits  $(N, M)$
- Modular approach for n-bits extension

$$N_i = N_{i+1} + \overline{a_i} b_i \overline{M_{i+1}}$$


$$M_i = M_{i+1} + a_i \overline{b_i} \overline{N_{i+1}}$$

Redundant terms

$a_i$	$b_i$	$N_{i+1}$	$M_{i+1}$	$N_i$	$M_i$
0	0	0	0	0	0
1	0	0	0	0	1
0	1	0	0	1	0
1	1	0	0	0	0
0	0	1	0	1	0
1	0	1	0	1	0
0	1	1	0	1	0
1	1	1	0	1	0
0	0	0	1	0	1
1	0	0	1	0	1
0	1	0	1	0	1
1	1	0	1	0	1
0	0	1	1	X	X
1	0	1	1	X	X
0	1	1	1	X	X
1	1	1	1	X	X

 
# Multiplexer

- A Mux selects one signal among  $2^n$  ( $D_i$ ) thanks to  $n$  address lines ( $S_j$ )
- For  $n = 1$ , two levels of NAND ports can easily implement it
- Any combinatorial function can be generated connecting the address lines to the variables and connecting 1 to  $D_i$  if the minterm  $m_i$  is present, 0 otherwise
- A Demux applies the inverse operation
- It can be used as decoder because it selects the output line  $D_i$  corresponding to the minterm  $m_i$



 
# Tristate

- It is used for developing bidirectional connections
- Many data buses are usually tristate because they are used to link devices that can be both source and sink of information
- A control line is used for putting the output in high-impedance




<i>A</i>	<i>C</i>	<i>B</i>
0	0	Z
1	0	Z
0	1	0
1	1	1

 


 
# Programmable Logic Array

- PLA consists of an AND array connected to an OR array
- Constant propagation delay
- It can build any sum of products
- The AND array can be fixed while the OR array is programmable
- Programmable logic-planes grow too quickly in size as the number of inputs is increased


  
# Field-Programmable Gate Array

- Programmable logic blocks linked by programmable interconnections
- Programmable Input and Output
- Configurable Logic Block can be either a combinatorial or a sequential circuit
- Look up tables are used to implement the truth table of a combinatorial function





# Exercise

- Design a circuit able to compare two 2-bit numbers at a time